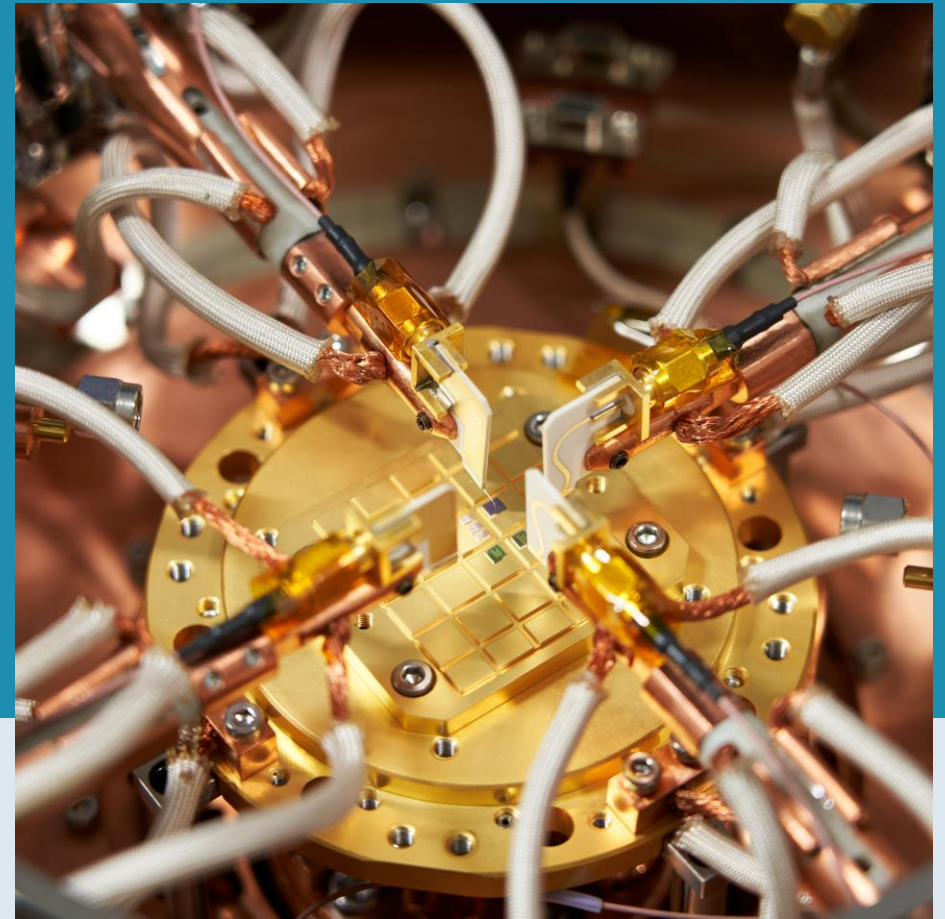


Design of Analog and Mixed-Signal Integrated Circuits B-KUL-H05E3A

The g_m/I_D methodology

Alberto Gatti, Jun Feng, Shuangmu Li, Prayag J. Wakale, Ir.
Filip Tavernier, Tim Piessens, Prof. Dr. Ir.
Department of Electrical Engineering (ESAT)



Outline



Motivation

- Scaling in CMOS
- Limitations of the Square Law model



The g_m/I_D design approach

- Basics
- Extracting model data



A design example

- The IGS

Outline



Motivation

- Scaling in CMOS
- Limitations of the Square Law model



The g_m/I_D design approach

- Basics
- Extracting model data



A design example


- The IGS

Why the scaling?

- 🔌 Silicon area (transistor density)
- 🔌 Speed (smaller parasitic caps)
- 🔌 Power: $P_d \sim CV_{DD}^2 \cdot f$
- 🔌 Analog is always essential...
 - Clock generation
 - Supply regulation
 - Sensor interfacing
- 🔌 ...but becomes challenging
 - Less intrinsic gain
 - Low $V_{DD} \rightarrow$ harder to reach high SNR
 - Worse $1/f$ noise

Moore's Law

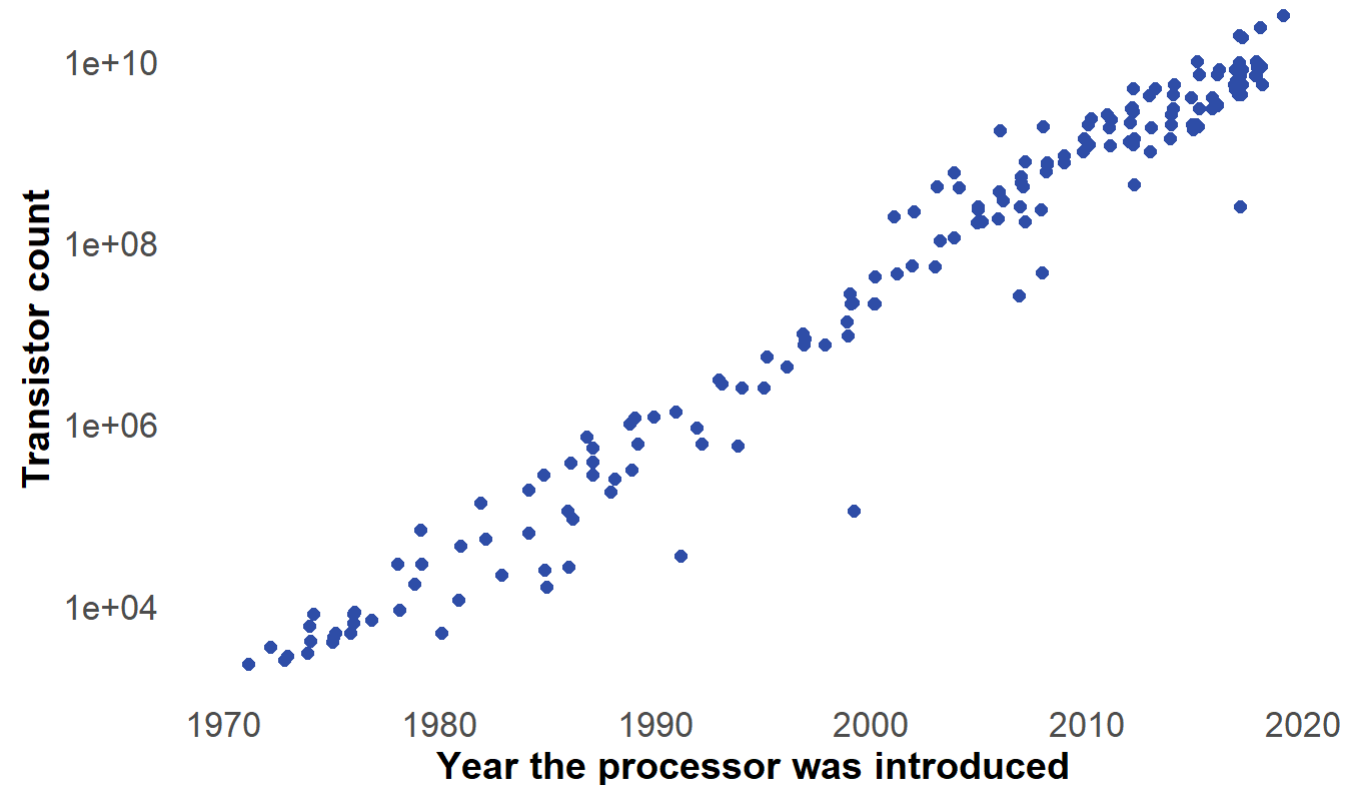CPU transistor count doubles roughly every two years



Source data: https://en.wikipedia.org/wiki/Transistor_count | Viz: Brian P. Dranka

Consequences of the scaling


- 🔧 Square Law model for a MOSFET in saturation:

$$I_D \approx \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

No longer suitable for design with nanoscale technologies!


- 🔧 Parameters like V_{th} and μ now depend on size, voltage, or both
 - Deviation from the square law equations!
- 🔧 Unfortunately, no simple equations available anymore
 - Hand calculations no longer possible/accurate for design

Square Law vs Modern CMOS

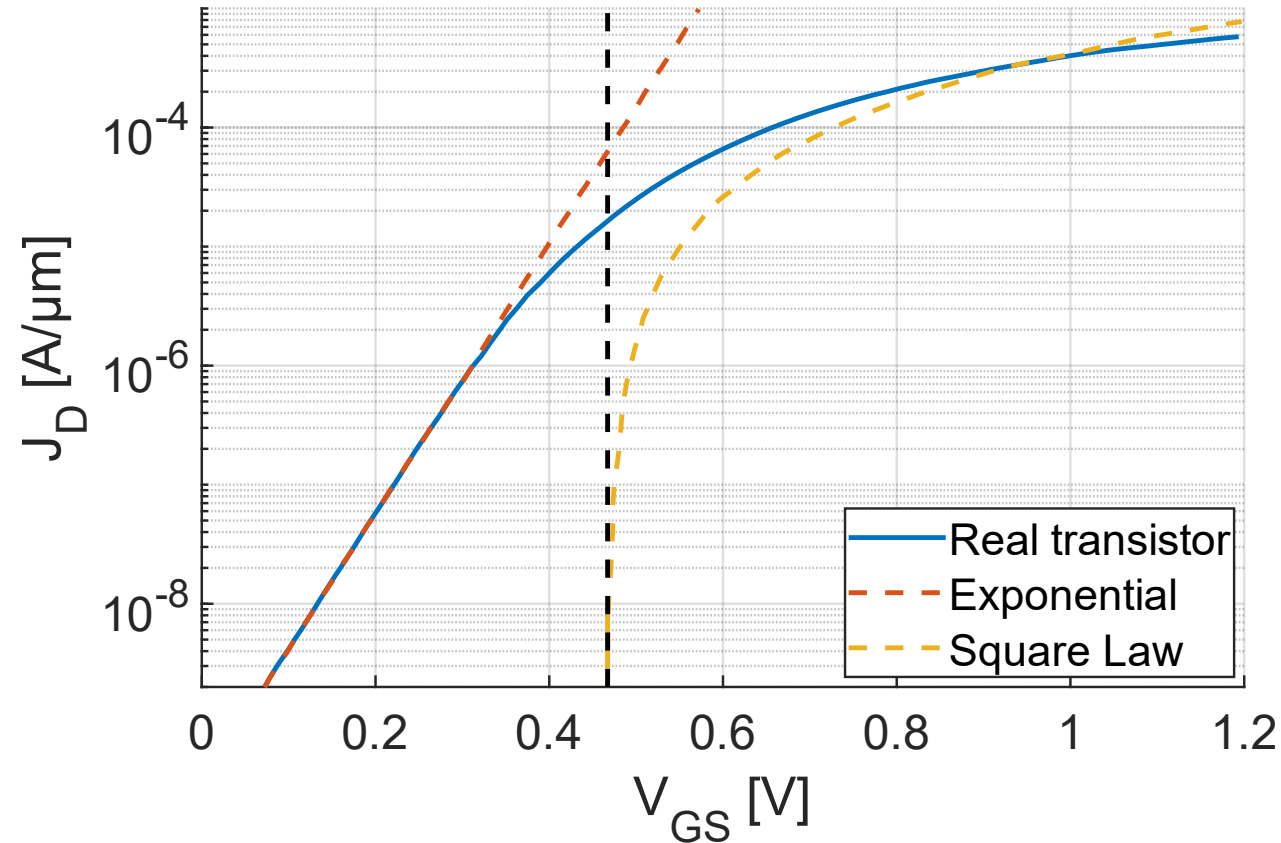

Current density of a minimum-length N-channel device in **65 nm** CMOS technology versus V_{GS} . The black vertical line marks the device threshold voltage.

Formulation of V_{th} in a modern model

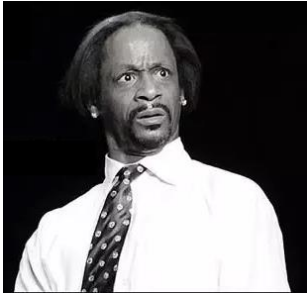

$$V_{th} = V_{TH0} + \left(K_{1ox} \sqrt{\Phi_s - V_{bseff}} - K_{11} \sqrt{\Phi_s} \right) \sqrt{1 + \frac{LPEB}{L_{eff}}} - K_{2ox} V_{bseff} + K_{1ox} \left(\sqrt{1 + \frac{LPE0}{L_{eff}}} \right) \sqrt{\Phi_s} \\ + (K_3 + K_{3B} \cdot V_{bseff}) \frac{TOXE}{W'_{eff} + W_0} \Phi_s - 0.5 \left[\frac{DVT0W}{\cosh\left(DVT1W \frac{L_{eff} W'_{eff}}{l_{tw}}\right) - 1} + \frac{DVT0}{\cosh\left(DVT1W \frac{L_{eff}}{l_t}\right) - 1} \right] (V_{bi} - \Phi_s) \\ - \frac{0.5}{\cosh\left(DSUB \frac{L_{eff}}{l_{t0}}\right) - 1} (ETA0 + ETAB \cdot V_{bseff}) V_{ds} - n v_t \cdot \ln\left(\frac{L_{eff}}{L_{eff} + DVT P_0 (1 + e^{-DVT P_1 \cdot V_{DS}})}\right)$$

- ⚙ The equation for the current factor $\beta = \mu C_{ox} \frac{W}{L}$ is only "slightly less complicated"...
- ⚙ A modern model has normally over 200 parameters

What to do now?



Option A: become a S.P.I.C.E. Monkey!

- Iterative, brainless tuning of design parameters
- Loss of insight into circuit operation
- Very time-inefficient
- Mostly ending with sub-optimal results



Option B: find a new link between high-level and transistor-level design



Some particularly clever designers went through option B for you...

- g_m/I_D methodology (Silveira, Flandre and Jespers)
- Inversion Coefficient (IC) methodology (Enz, Krummenacher, and Vittoz)
- Several other short-channel methodologies

Outline



Motivation

- Scaling in CMOS
- Limitations of the Square Law model



The g_m/I_D design approach

- Basics
- Extracting model data




A design example

- The IGS

The inversion level

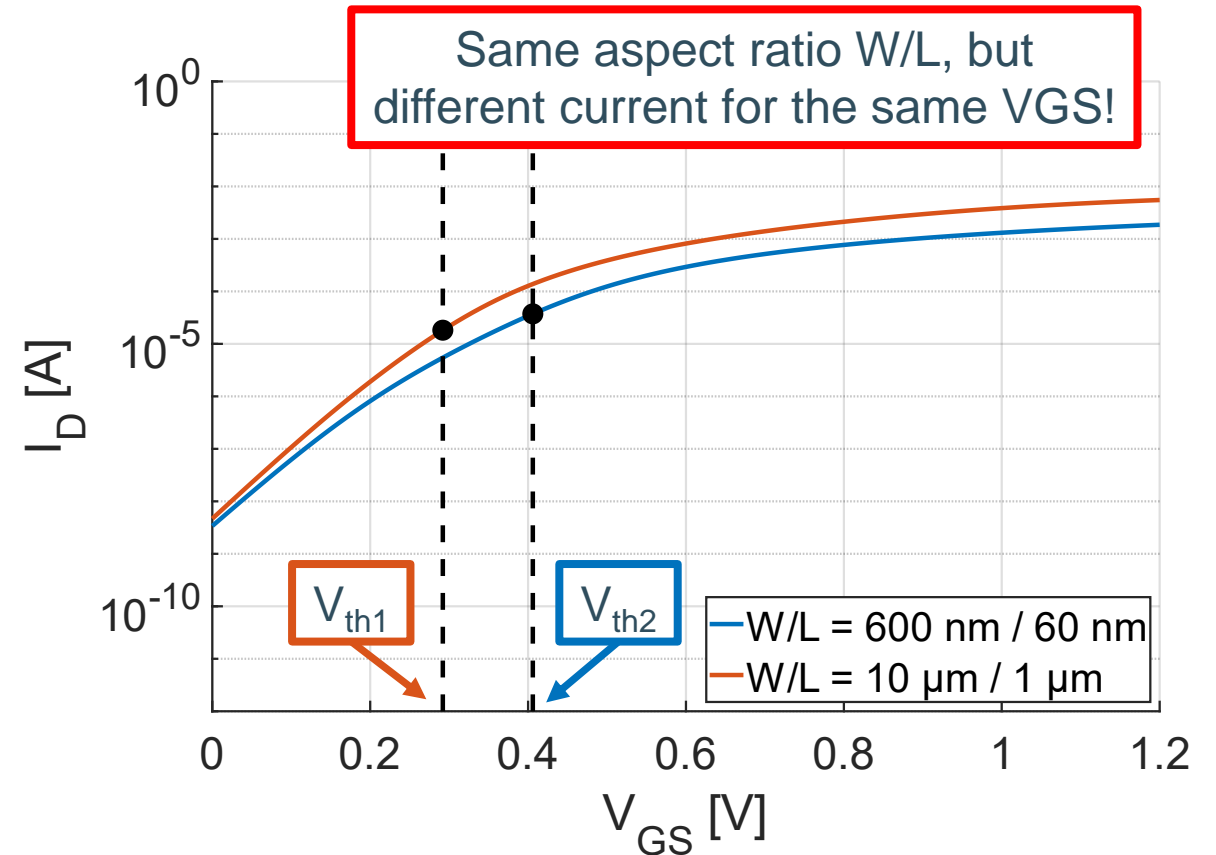- $V_{OV} = V_{GS} - V_{th}$ no longer useful
 - V_{th} is not constant!
 - Also, no unique definition of V_{th} ...
- Transistor behavior depends on the **inversion level**
 - Density of carriers in the channel
 - (Inversion layer)
- Two transistors with the same V_{GS} may have different inversion levels
 - Because their V_{th} may be different!



Example data for a real **65 nm** CMOS technology.

The transconductance efficiency g_m/I_D

• $\frac{g_m}{I_D} = \frac{1}{nU_T} \frac{1}{q_{i+1}} [V^{-1}]$


- n = subthreshold factor
- U_T = thermal voltage (kT/q)
- q_i = normalized mobile charge density

• $\rho = \frac{g_m/I_D}{\max(g_m/I_D)}$

• **Proxy for the inversion level**



- Weak inversion $\sim [\rho < 0.8]$
- Moderate inversion $\sim [0.8 < \rho < 0.2]$
- Strong inversion $\sim [\rho > 0.2]$

• Amount of g_m for a given I_D

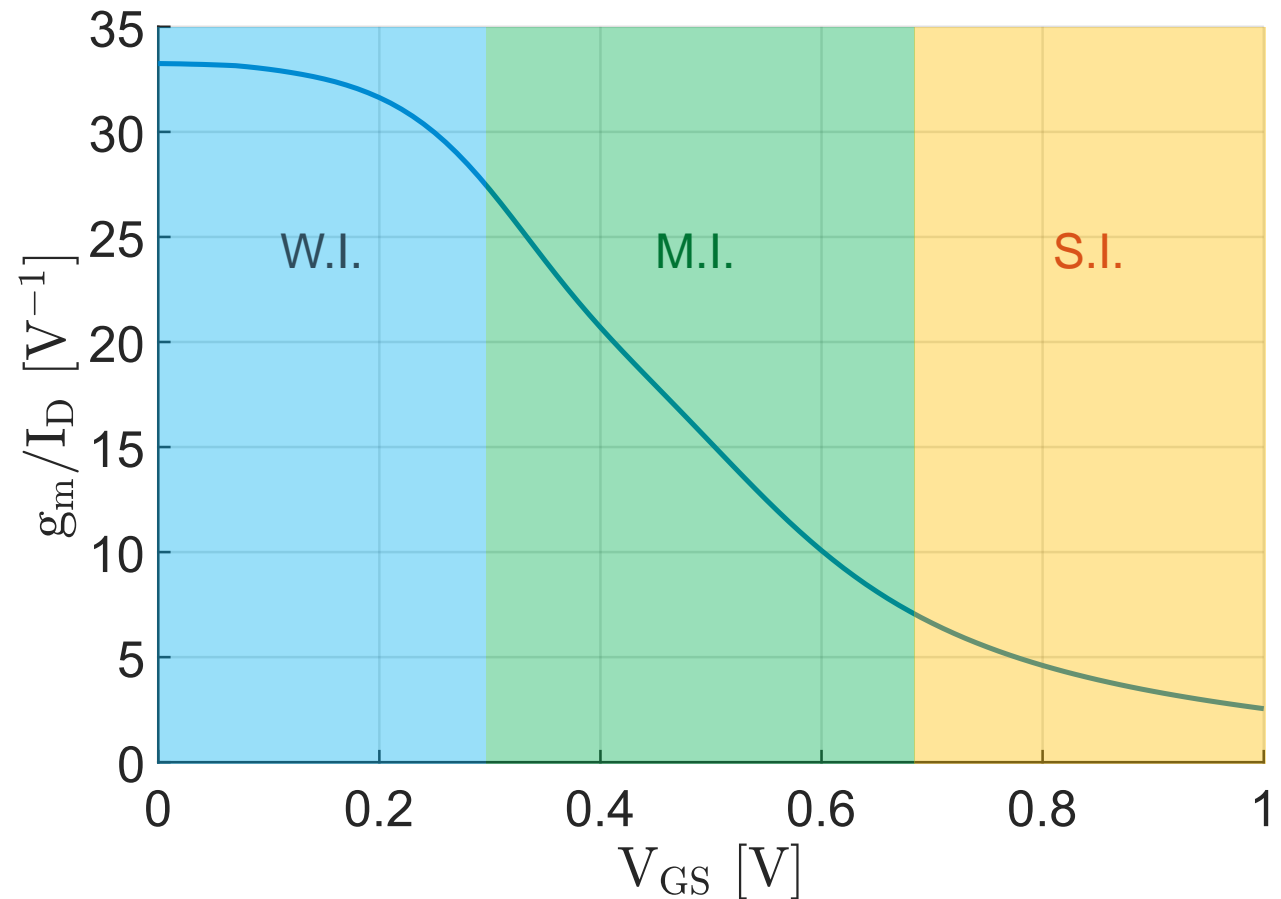

Example data for an N-channel device with $L = 180$ nm in the 45 nm GPDK.

Transit Frequency and Intrinsic Gain

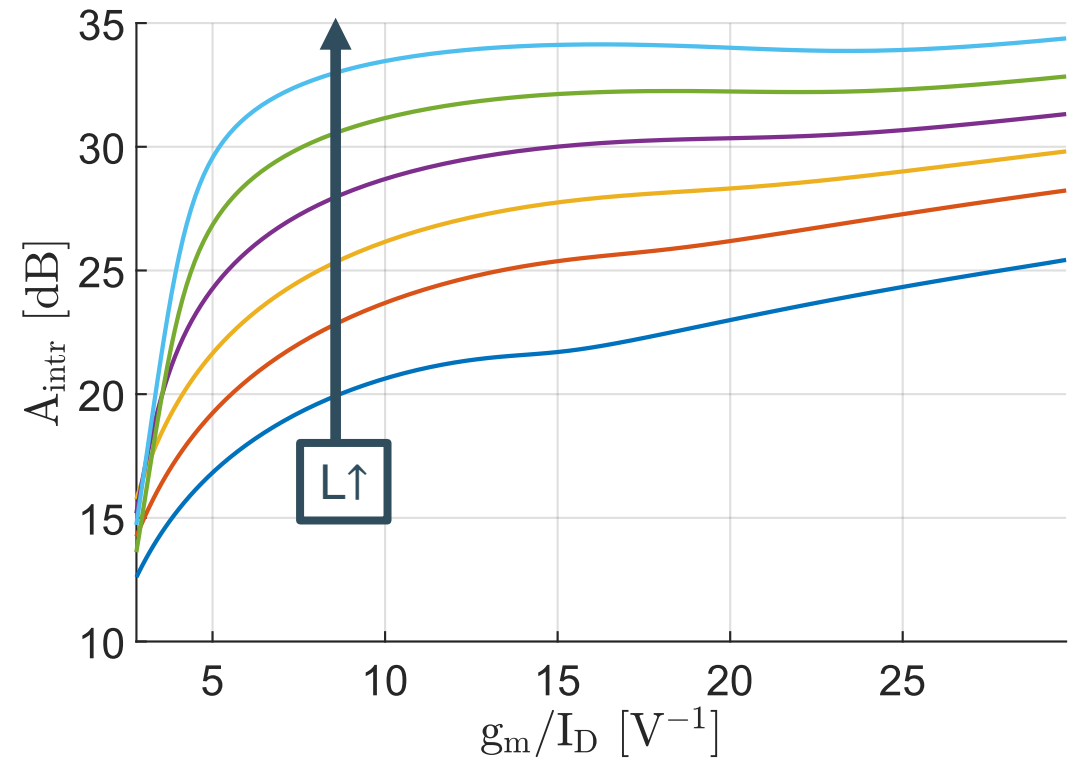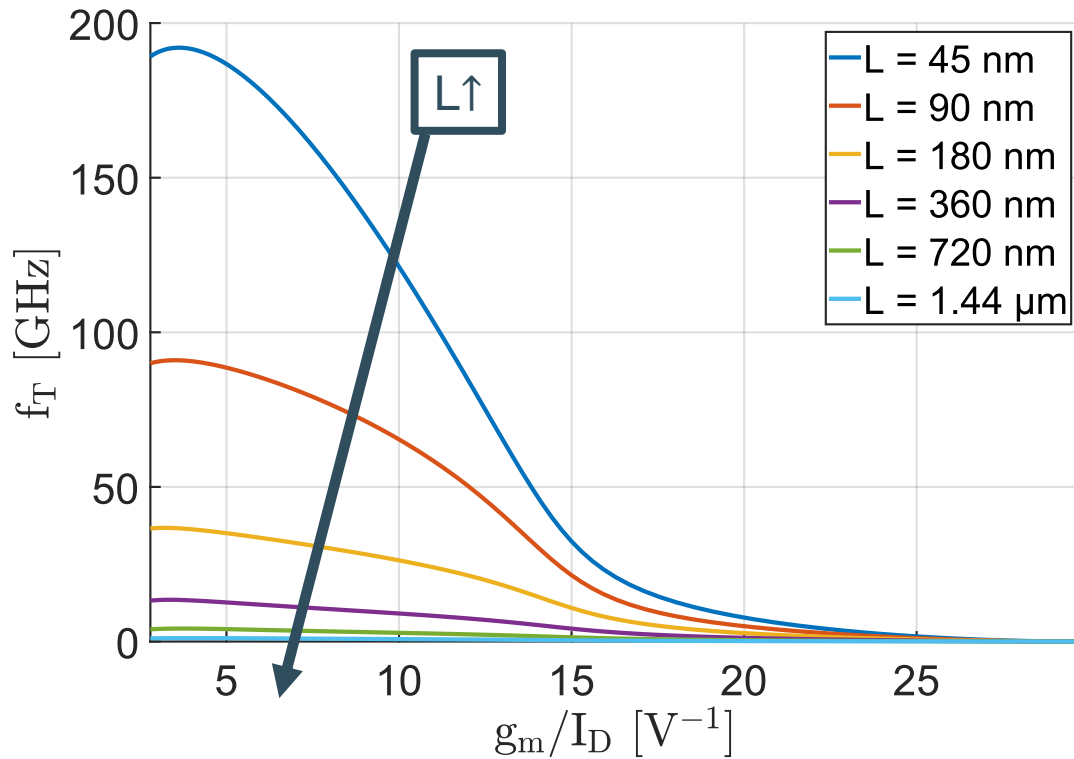

Transit Frequency f_T (left) and low-frequency intrinsic gain A_{intr} (right) versus g_m/I_D for several values of the channel length L . Curves for an N-channel device in the **45 nm GPDK**. $W = 40 \mu m$, $V_{DS} = 500 mV$.



The Drain Saturation Voltage

- The drain saturation voltage V_{Dsat} can be expressed as:

$$V_{Dsat} = \frac{2}{g_m/I_D}$$


- In weak inversion, $V_{Dsat} \rightarrow 2nU_T$
- In strong inversion, $V_{Dsat} \approx V_{GS} - V_{th}$
 - No longer true in deep strong inversion because of mobility degradation

The g_m/I_D Testbench

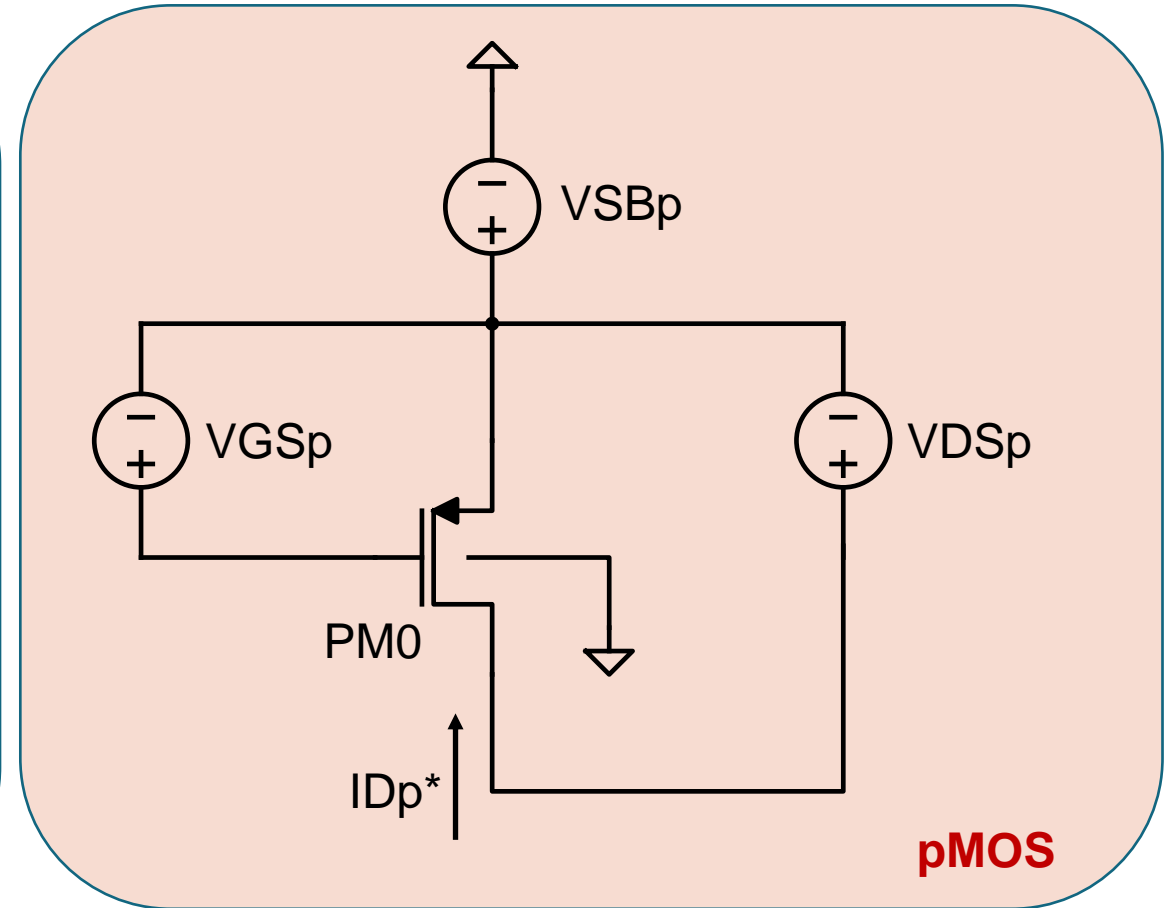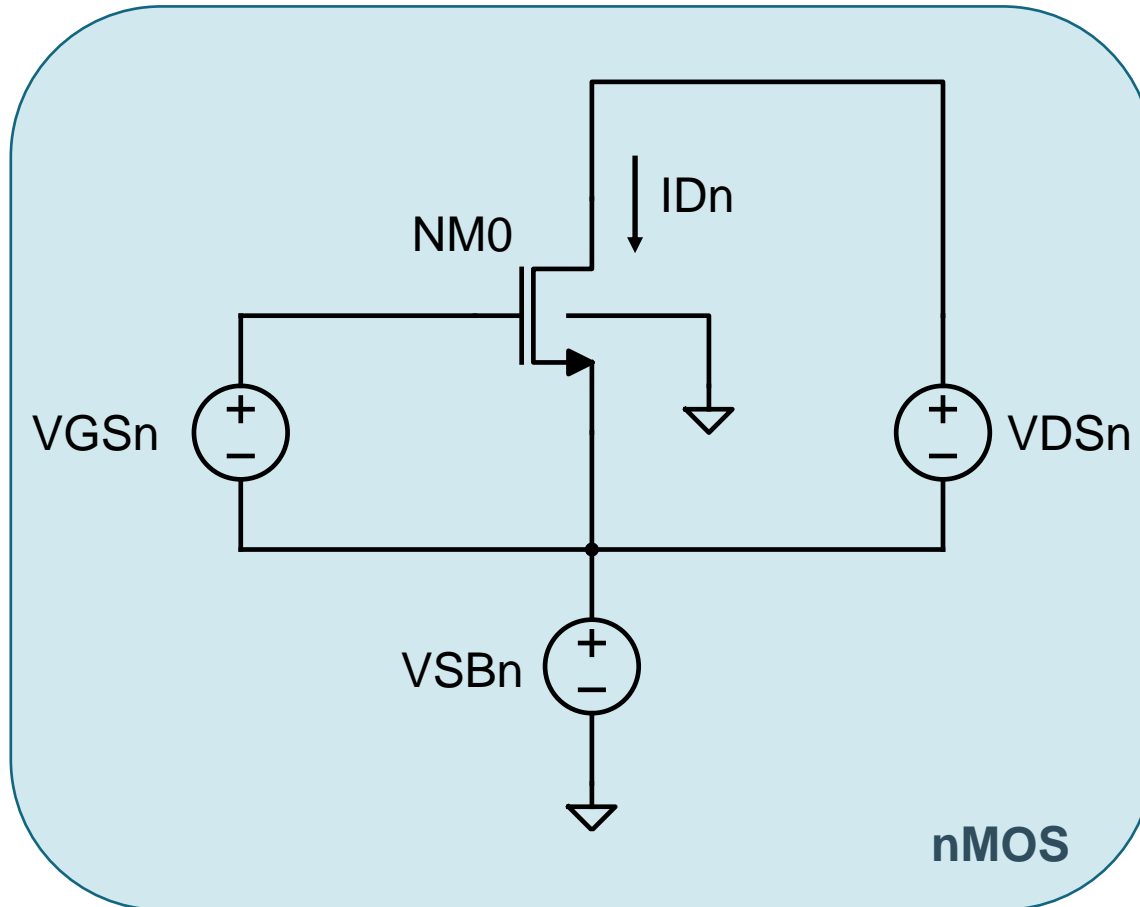

Use of the g_m/I_D Testbench

- Cellname: *gmoverid_plots*
 - Already in the library we provided!
- Open the *maestro* view in ADE Explorer
- pMOS voltages are negative
 - Remember to use a negative step in sweeps
- Channel width $W = NF \cdot WF$
 - W = device width (design)
 - NF = number of fingers
 - WF = finger width
- A finger width of **0.5...2 μm** is a good compromise (for this node)*
 - In real circuits, NF and WF are chosen to optimize layout too

 


The screenshot shows the 'Design Variables' window. The parameters are listed in a table:

Variable	Value
Ln	45n
NFn	20
WFn	1u
VGSn	500m
VDSn	500m
VSBn	0
Lp	45n
NFp	20
WFp	1u
VGSp	-500m
VDSp	-500m
VSBp	0

Use of the g_m/I_D Testbench

Select plot mode (Append, Replace, ...)

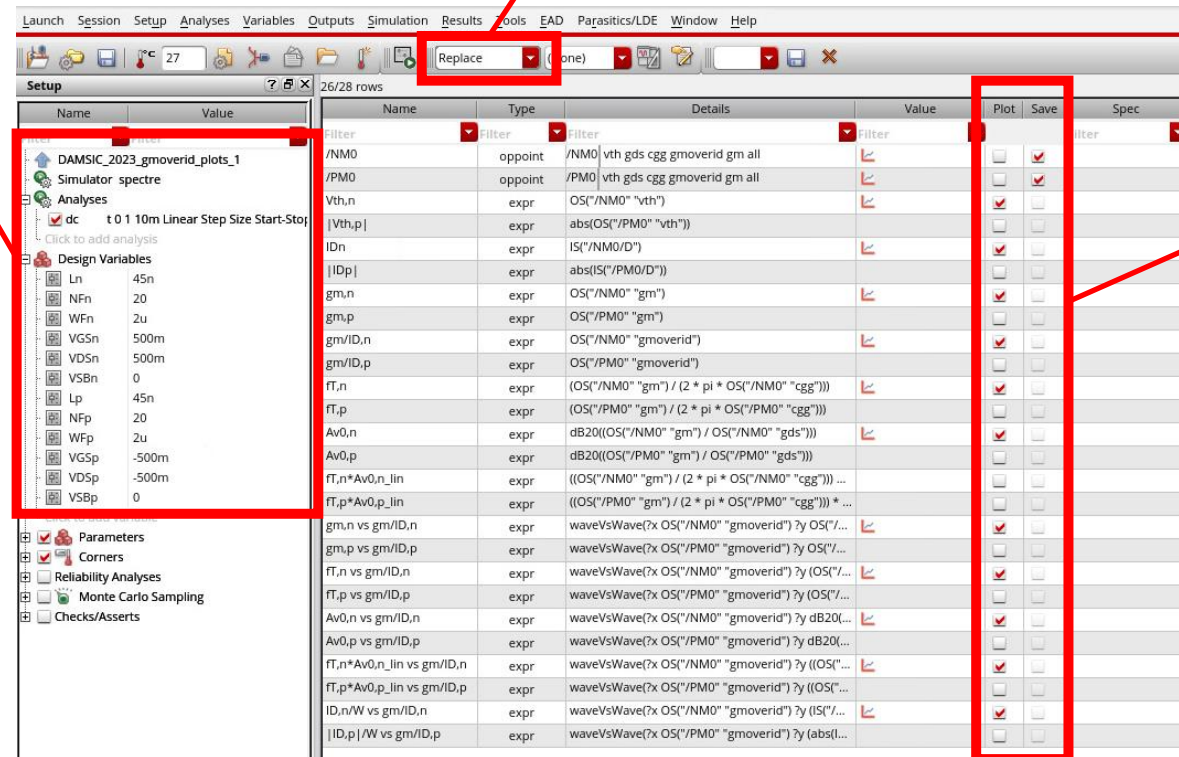Change the DC sweep
and/or execute
parametric simulations







Plot only what you need
(nMOS or pMOS, specific
expressions, etc.)

General hint: if you need/want to plot more signals/expressions, use the Calculator (*Tools* → *Calculator*) and the built-in Expression Builder of ADE Explorer/Assembler

Design tips (1)

- g_m/I_D is weakly dependent on W and V_{DS}
- I_D/W is weakly dependent on W^* and V_{DS}
- However, for the same value of g_m/I_D but different values of W and/or V_{DS} , the value of other analog FoMs (g_m , f_T , ...) can change!
 - Try to see how/if the plots change by varying W , L , V_{DS} and V_{BS}
- It's a good idea to double-check with the help of the g_m/I_D testbench
 - with W closer to the "final" size and the V_{DS} you expect in your circuit
- **Never forget to check that the devices are in saturation!**
 - By default, the g_m/I_D testbench sets $V_{DSn} = V_{DD}/2$ and $V_{DSp} = -V_{DD}/2$
 - This enforces saturation up to $\sim g_m/I_D = 4$ and it's a good starting point for design

Design tips (2)

-  Try to plot A_{intr} sweeping the channel length L
 - V_{GS} can be fixed to 500-600 mV for this purpose, or parametrized
 - After a certain value of L , increasing it further will have a diminishing return
-  Have a look at the $A_{intr} \cdot fT$ plot(s)
 - Useful when you need a fair compromise between gain and speed
-  Try replacing the devices with LVT/HVT ones
 - For the testbench to work, they must use the same names NM0/PM0
-  Add your own expressions/plots!

Outline



Motivation

- Scaling in CMOS
- Limitations of the Square Law model



The g_m/I_D design approach

- Basics
- Extracting model data



A design example

- The IGS

A generic sizing flow

NOT a magical
recipe for design!

1. Determine g_m (from design specifications)
2. Pick L :
 - Short channel \rightarrow high speed, small area;
 - Long channel \rightarrow high intrinsic gain, improved matching...
3. Pick g_m/I_D :
 - Large $g_m/I_D \rightarrow$ low power, large signal swing (low V_{Dsat});
 - Small $g_m/I_D \rightarrow$ high speed, small area.
4. Determine I_D (using g_m and g_m/I_D)
5. Determine W (using the I_D/W plot)

Design example: Intrinsic Gain Stage

• Ideal version of a CS stage

• Specifications:



- $f_C^* = 1 \text{ GHz}$ with $C_L = 1 \text{ pF}$
- $V_{DS} = 500 \text{ mV}$, $V_{SB} = 0 \text{ V}$
- $L = L_{min}$
- $g_m/I_D = 10$

• We neglect junction capacitances and assume $C_{db} \ll C_L$

• Under these assumptions, the frequency response is well-approximated by the expression:

$$A_V(j\omega) = \frac{v_{OUT}}{v_{IN}} \cong \frac{A_{v0}}{1 + j \frac{\omega}{\omega_{-3dB}}}$$

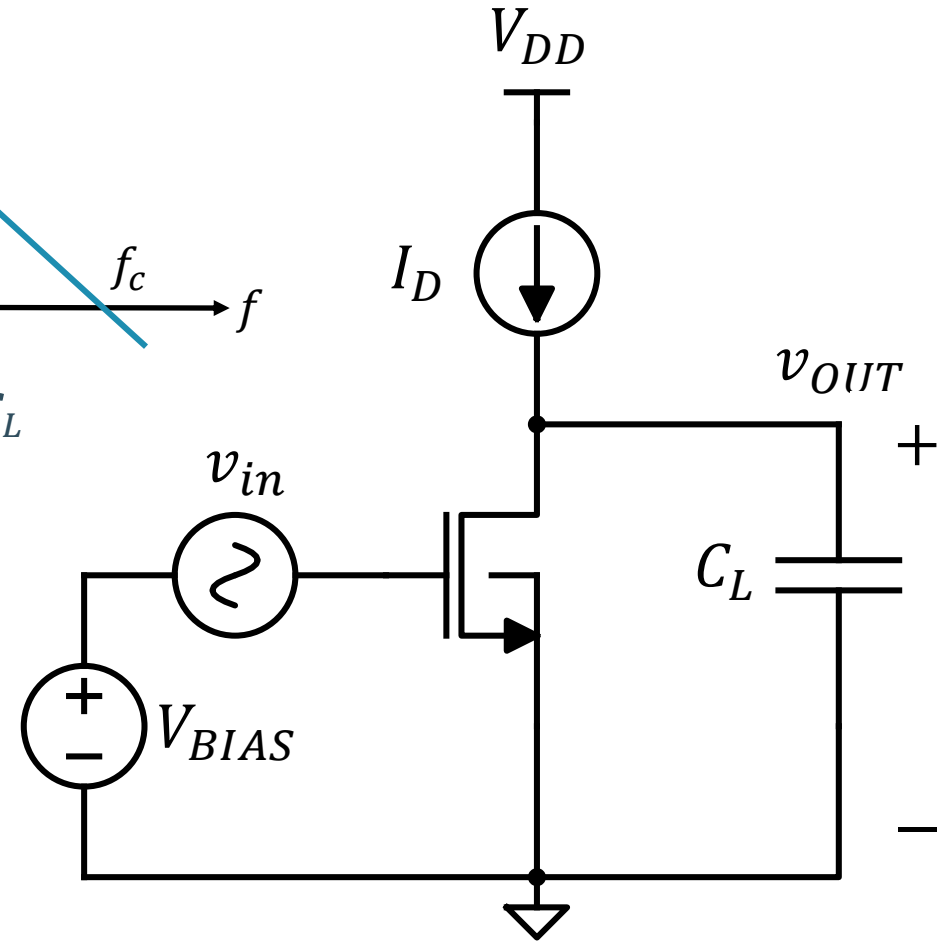 - $A_{v0} = -A_{intr} = -g_m/g_{ds}$
- $\omega_{-3dB} = \frac{g_{ds}}{C_L} \rightarrow f_{-3dB} = \frac{g_{ds}}{2\pi C_L}$



Design example: Intrinsic Gain Stage (2)

- We know (GBW...) that $f_c = \frac{g_m}{2\pi C_L}$
 - Therefore $g_m = 2\pi f_c C_L \cong 6.28 \text{ mS}$
- Specs are asking for minimum length, so $L = L_{min} = 45 \text{ nm}$
- Since g_m/I_D is set to 10, we have $I_D = \frac{g_m}{g_m/I_D} = 628 \text{ }\mu\text{A}$
 - Note that $g_m/I_D = 10 \rightarrow V_{Dsat} = 200 \text{ mV}$
 - If the output voltage goes below -300 mV from the quiescent V_{DS} , the device will leave saturation
- To calculate the value of W , we will use the I_D/W vs g_m/I_D plot
 - Already included in the g_m/I_D testbench

Design example: Intrinsic Gain Stage (3)

From the plot, we get:

$$I_D/W \cong 55 \text{ A/m}$$


We can finally compute:

$$W = \frac{I_D}{I_D/W} \cong 11.5 \text{ } \mu\text{m}$$

- $NF = 10$ and $WF = 1.15 \text{ } \mu\text{m}$ will be fine

We finally have our sizing:

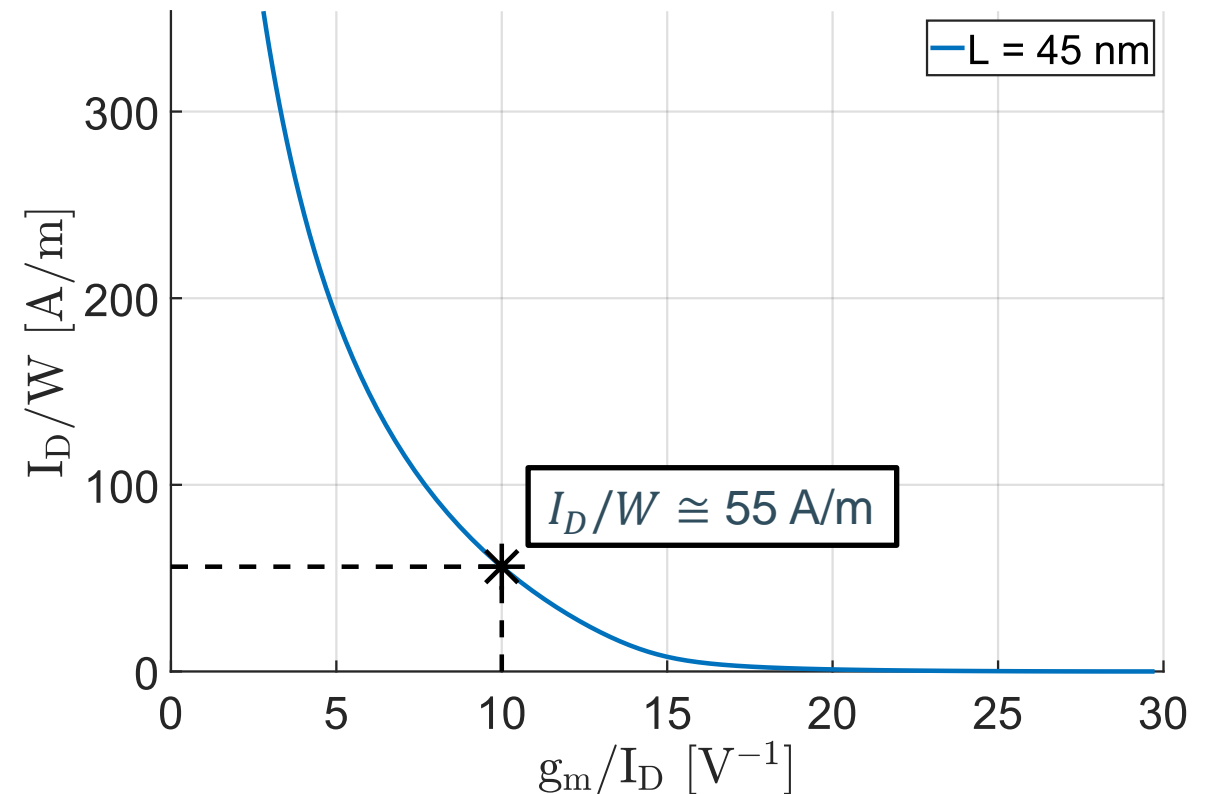
- $W = 10 * 1.15 \text{ } \mu\text{m}$
- $L = 45 \text{ nm}$
- $I_D = 628 \text{ } \mu\text{A}$



Verification of the IGS sizing

- To check the results, a testbench is available
 - Cell *IGS_Testbench* in the DAMSIC library
 - You can repeat the same exercise with the pMOS version

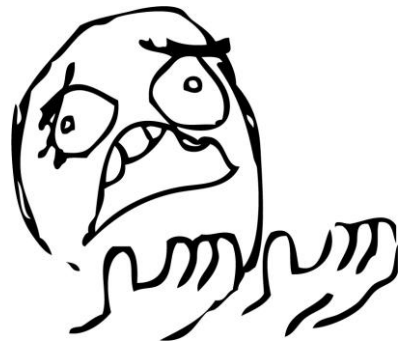- Let's put in the numbers...
- ...and we fail to reach the specs.
- Why?




Name	Type	Details	Value	Plot	Save	Spec
/NM0	oppo	/NM0 all		<input type="checkbox"/>	<input checked="" type="checkbox"/>	
/PM0	oppo	/PM0 all		<input type="checkbox"/>	<input checked="" type="checkbox"/>	
gm,n	expr	OP("/NM0" "gm")	6.3m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 6.28m
gm,p	expr	OP("/PM0" "gm")		<input type="checkbox"/>	<input type="checkbox"/>	> 6.28m
gm/ID,n	expr	OP("/NM0" "gmoverid")	10.03	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gm/ID,p	expr	OP("/PM0" "gmoverid")		<input type="checkbox"/>	<input type="checkbox"/>	
VGSn	expr	VDC("/Vinn")	668.3m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
VGSp	expr	(VDC("/Vinp") - VDC("/vdd!"))		<input type="checkbox"/>	<input type="checkbox"/>	
VDSn	expr	VDC("/Voutn")	500m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> (2 / calcVal("gm/ID,n"))
VDSp	expr	(VDC("/Voutp") - VDC("/vdd!"))		<input type="checkbox"/>	<input type="checkbox"/>	< (-1 * (2 / calcVal("gm/ID,p")))
Av ,n	expr	dB20(mag(VF("/Voutn")))		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
Av ,p	expr	dB20(mag(VF("/Voutp")))		<input type="checkbox"/>	<input type="checkbox"/>	
UGFn	expr	cross(dB20(mag(VF("/Voutn"))) 0)	993.3M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 1G
UGFp	expr	cross(dB20(mag(VF("/Voutp"))) 0)		<input type="checkbox"/>	<input type="checkbox"/>	> 1G
Av0,n	expr	value(dB20(mag(VF("/Voutn"))) 1)	20.85	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 0
Av0,p	expr	value(dB20(mag(VF("/Voutp"))) 1)		<input type="checkbox"/>	<input type="checkbox"/>	> 0

Inclusion of the parasitic capacitance

- ⚙️ We neglected the parasitic capacitance at the output node
- ⚙️ We can compute C_{Par} from the UGF value:

$$f_c = \frac{g_m}{2\pi(C_L + C_{Par})} \rightarrow C_{Par} \cong 9.5 \text{ fF}$$

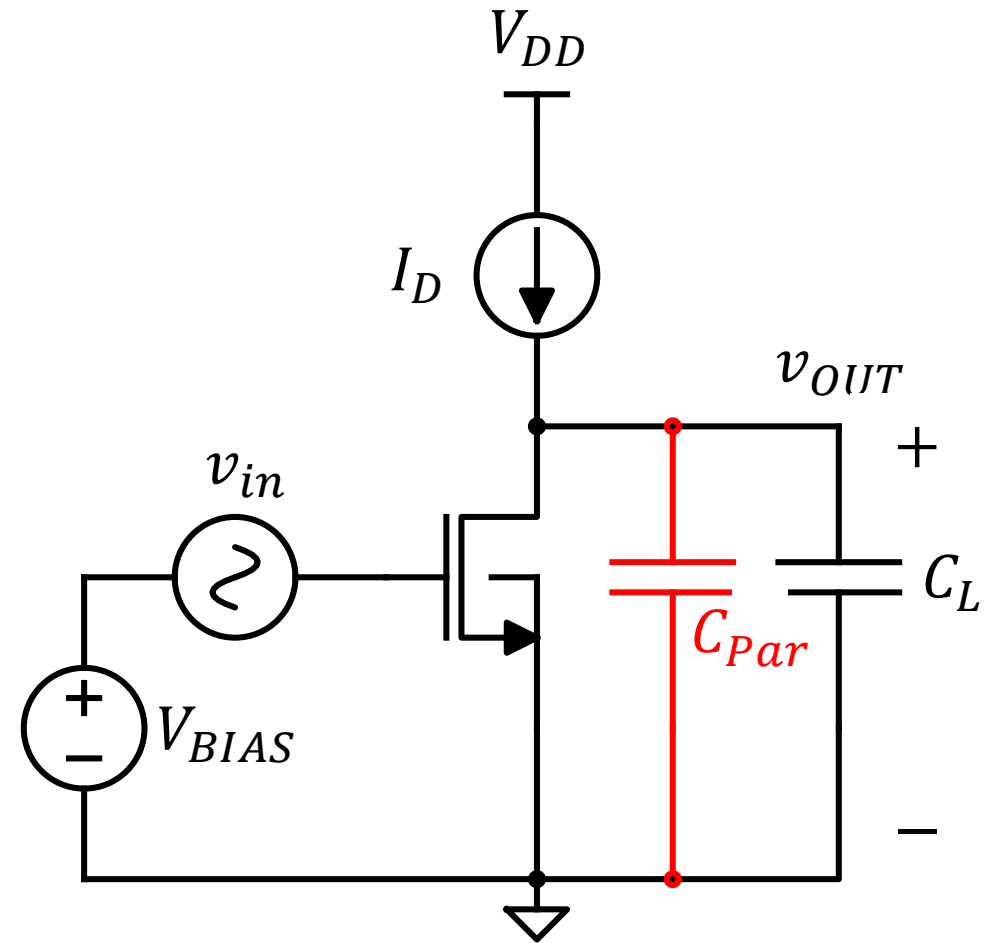- ⚙️ We repeat the design procedure replacing C_L with $C_{TOT} = C_L + C_{Par}$
 - If the transistor size change considerably, we may need multiple iterations



Verification of the IGS resize



New values:

- $W = 10 \times 1.15 \text{ } \mu\text{m}$
- $L = 45 \text{ nm}$
- $I_D = 634 \text{ } \mu\text{A}$



Now we have reached the specs!



We just needed a bit more current

- Pretty obvious, right?

Name	Type	Details	Value	Plot	Save	Spec
/NM0	oppooint	/NM0 all		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
/PM0	oppooint	/PM0 all		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	
gm,n	expr	OP("/NM0" "gm")	6.344m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 6.28m
gm,p	expr	OP("/PM0" "gm")		<input type="checkbox"/>	<input type="checkbox"/>	> 6.28m
gm/ID,n	expr	OP("/NM0" "gmoverid")	9.99	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gm/ID,p	expr	OP("/PM0" "gmoverid")		<input type="checkbox"/>	<input type="checkbox"/>	
VGSn	expr	VDC("/Vinn")	669.4m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
VGS p	expr	(VDC("/Vinp") - VDC("/vdd!"))		<input type="checkbox"/>	<input type="checkbox"/>	
VDSn	expr	VDC("/Voutn")	500m	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> (2 / calcVal("gm/ID,n"))
VDS p	expr	(VDC("/Voutp") - VDC("/vdd!"))		<input type="checkbox"/>	<input type="checkbox"/>	< (-1 * (2 / calcVal("gm/ID,p")))
Av ,n	expr	dB20(mag(VF("/Voutn")))		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
Av ,p	expr	dB20(mag(VF("/Voutp")))		<input type="checkbox"/>	<input type="checkbox"/>	
UGFn	expr	cross(dB20(mag(VF("/Voutn")) 0)	1G	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 1G
UGFp	expr	cross(dB20(mag(VF("/Voutp")) 0)		<input type="checkbox"/>	<input type="checkbox"/>	> 1G
Av0,n	expr	value(dB20(mag(VF("/Voutn")) 1)	20.83	<input checked="" type="checkbox"/>	<input type="checkbox"/>	> 0
Av0,p	expr	value(dB20(mag(VF("/Voutp")) 1)		<input type="checkbox"/>	<input type="checkbox"/>	> 0

Design tips (3)

- The maximum frequency of interest (f_c in the previous example) sets a limit on the choice of L
 - As a conservative rule of thumb*, circuits operate predictably only **up to $f_T/10$**
- Be smart when you choose g_m/I_D
 - Remember that $V_{Dsat} = 2 / \left(\frac{g_m}{I_D} \right) \rightarrow$ places a limit on signal swing
 - For example, requiring $V_{Dsat} = 150$ mV means $g_m/I_D = 13.33$ V⁻¹
- **Models are not perfect**
 - This is essentially why a phase margin of a few degrees is not enough to ensure stability...
 - Always keep some margin on the specifications you want to achieve
 - Mismatch/PVT simulations are only as good as the silicon-proven reliability of the process
 - Foundries periodically update PDKs with improvements to the models and to the process, even after years
- Don't go crazy over differences of ± 1 dB in open-loop gain or ± 1 mV in bias voltages...
 - ... the circuit will never behave so precisely anyway, in reality
 - High accuracy is achieved with feedback loops and/or other techniques (trimming, calibration, ...)

References

- P. R. Kinget, "Scaling analog circuits into deep nanoscale CMOS: Obstacles and ways to overcome them," 2015 IEEE Custom Integrated Circuits Conference (CICC).
- A.-J. Annema, B. Nauta, R. van Langevelde, and H. Tuinhout, "Analog circuits in ultra-deep-submicron CMOS," IEEE Journal of Solid-State Circuits, vol. 40, no. 1, pp. 132–143, Jan. 2005.
- D. W. Liu, D. X. Jin, D. Kanyu, D. J. He, D. Xuemei, and C. Hu, "BSIM 4.5.0 Mosfet Model User's Manual," EECS Department, University of California, Berkeley, 2005. [Online]. Available: <http://bsim.berkeley.edu/models/bsim4/>
- W. Sansen, "Minimum Power in Analog Amplifying Blocks: Presenting a Design Procedure," IEEE Solid-State Circuits Mag., vol. 7, no. 4, pp. 83–89, 2015.
- F. Silveira, D. Flandre and P. G. A. Jespers, "A gm/ID based methodology for the design of CMOS analog circuits and its application to the synthesis of a silicon-on-insulator micropower OTA," in IEEE Journal of Solid-State Circuits, vol. 31, no. 9, pp. 1314-1319, Sept. 1996.
- J. Ou and P. M. Ferreira, "A gm/ID-Based Noise Optimization for CMOS Folded-Cascode Operational Amplifier," in IEEE Transactions on Circuits and Systems II: Express Briefs, vol. 61, no. 10, pp. 783-787, Oct. 2014.
- W. Steyaert and P. Reynaert, "Layout optimizations for THz integrated circuit design in bulk nanometer CMOS," in 2017 IEEE Compound Semiconductor Integrated Circuit Symposium (CSICS), Oct. 2017, pp. 1–4.
- Y. Tsividis, C. McAndrew, "Operation and Modeling of the MOS Transistor," Oxford University Press, 2010.
- C. C. Enz and E. A. Vittoz, "Charge-based MOS Transistor Modeling: The EKV Model for Low-Power and RF IC Design", John Wiley & Sons, 2006.
- Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, Robert G. Meyer, "Analysis and Design of Analog Integrated Circuits," 5th edition, Wiley, 2009.
- W. Sansen, "Analog Design Essentials," Springer, 2006.
- P. Jespers, "The gm/ID Methodology, A Sizing Tool for Low-voltage Analog CMOS Circuits," Springer, 2010.
- P. Jespers, B. Murmann, "Systematic Design of Analog CMOS Circuits," Cambridge University Press, 2017.
- T.H. Lee, "The Design of CMOS Radio-Frequency Integrated Circuits", 2nd ed. Cambridge University Press, 2004.
- D. Binkley, "Tradeoffs and Optimization in Analog CMOS Design," Wiley, 2008.
- D. Stefanovic and M. Kayal, "Structured Analog CMOS Design," Springer, 2008.

Today's Session

 Work on system level understanding, use ideal OTA

- If you are fast, go on with transiter level design

 Check out the report template

 Seminar at 11, we stop at ~10:50