




# Design of Analog and Mixed-Signal Integrated Circuits B-KUL-H05E3A

## Simulation Demo's STB, PSS+PNOISE, PAC

Alberto Gatti, Rico J. Maestro, Jun Feng, Shuangmu Li, Prayag J. Wakale Prof. Filip Tavernier

Departement Elektrotechniek (ESAT)

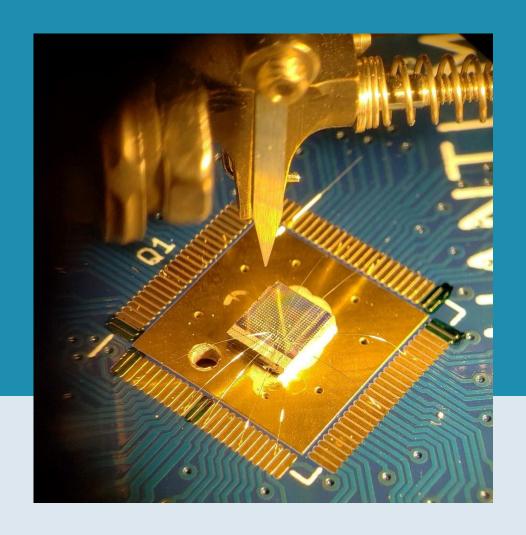

#### Overview

- These slides show how to setup simulations for
  - 1. Stability → STB simulation
  - 2. Noise → PSS + PNOISE simulation
  - 3. Accuracy → PAC simulation
- We also provide some demo's so you can try for yourself

Note: we skip basic transient and AC simulations, these are crucial for stability and accuracy simulations though! See syllabus appendix, if needed



## STABILITY LOOP GAIN SIMULATION SETUP AND DEMO



#### Stability simulation: what's needed?

- An STB analysis assumes a single operating point
  - "Steady-state solution"


So, you must force your switch-cap system in a single state first

- In this system, you should force it into the sample phase
  - Hardest to get stable (unity feedback)
  - Also, the other phase doesn't bias the input of the OTA in steady-state...


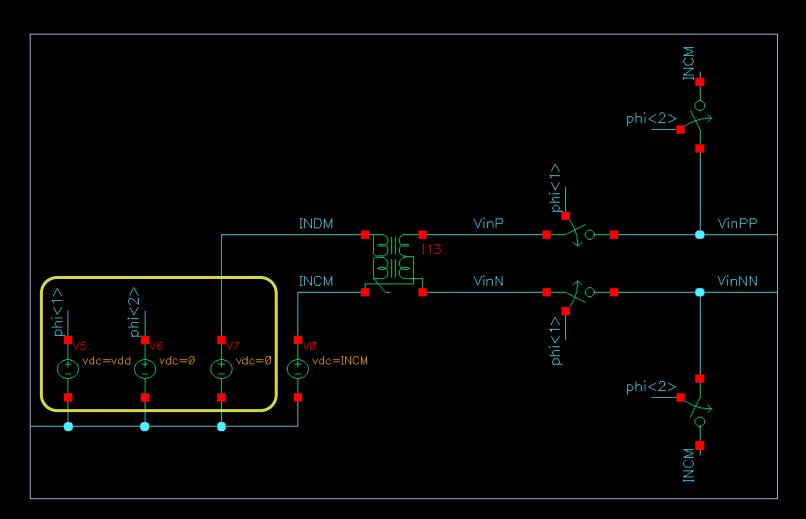
#### Modifying the testbench for STB

- Copy the standard transient testbench
- Modify to force the sampling phase
- 3. Make the differential input 0V too, since this is not an AC or transient simulation





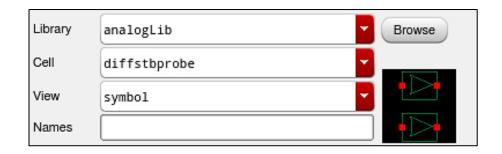
#### diffstbprobe


- You also need to insert a "diffstbprobe"
  - Differential stability probe



In this example, we have an ideal 2-pole OTA which doesn't have common-mode feedback. There's only one differential feedback loop.





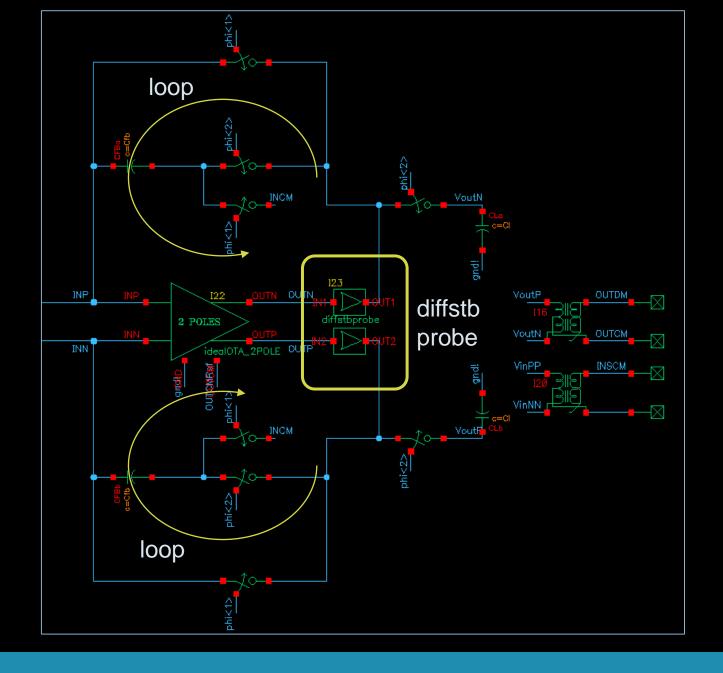


## Modifying the testbench for STB

- Easiest location here:output of the OTA
- In the future you will have multiple feedback loops, resulting in multiple options



#### Simulation setup

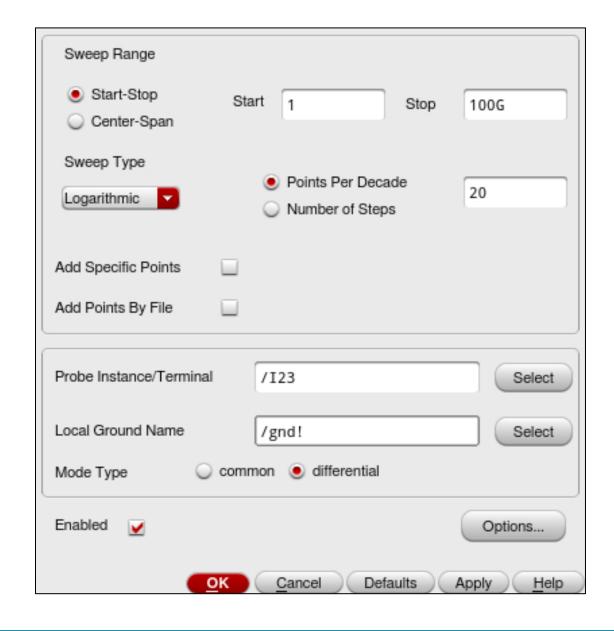
- 1. Launch new) ADE Explorer view
- Add analysis: choose "stb" and pick a frequency sweep (to get bode plot of loop gain)
- 3. "Probe Instance" = the diffstbprobe you inserted
- 4. Local Ground Name = /gnd!
- 5. Finish setting up design variables → run!




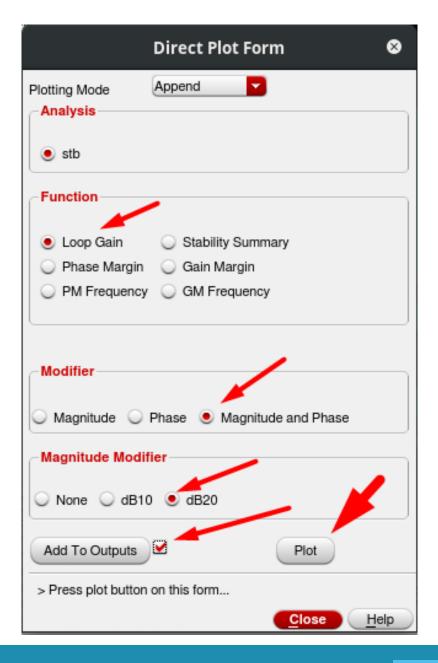
#### Plotting STB's result

- In ADE: Results > Direct Plot > Main
   Form ...
- You can plot either Loop Gain bode plot, or just print the Stability Summary
- 3. Check "Add To Outputs" to push the expression to ADE, so you can re-use ©
  - You could do the same for Phase Margin or Gain Margin options of the Direct Plot Form







#### Demo 1: "demo\_SCAMPLIFIER\_STB\_TB"

- We've modified the testbench schematic as described
- We've replaced the idealOTA by a 2-pole idealOTA
  - It has an extra gm-C stage, where gm = 1 and C = CP2 (variable)
  - So, an extra pole will be placed at roughly  $1/(2\pi^*CP2)$
- The maestro view is already setup with design variables and a second pole that is close to the dominant unity-gain frequency
  - What is the phase margin?
  - Could you place the same OTA in a transient to see the predicted instability?



#### Demo 1 example

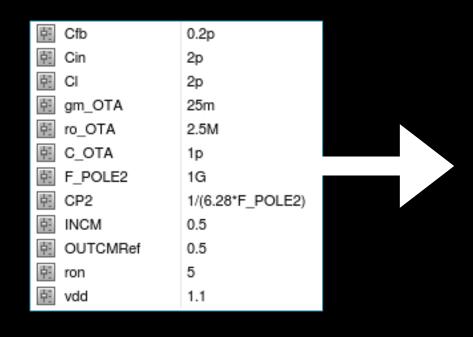

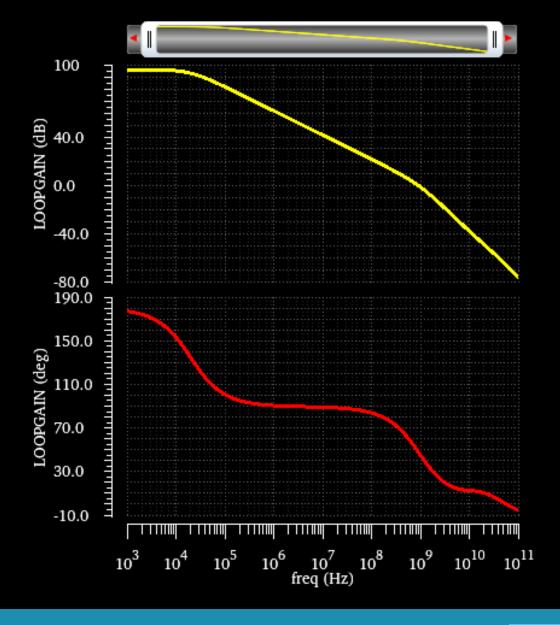



### PSS + PNOISE SIMULATION SETUP AND DEMO



#### PSS simulation and setup (1)


- Periodic steady state analysis
- It computes the steady states vs. time in your circuit within one period
   (normal AC sim = just one steady state)

- To keep simulation time low, we disable the input sine wave in the schematic → the "period" will be limited by the clock
  - Trade-off for accuracy, generally OK for this kind of design in DAMSIC
  - You can set the input sine wave frequency to 0 Hz, Cadence treats it as DC source then



### PSS setup (2)

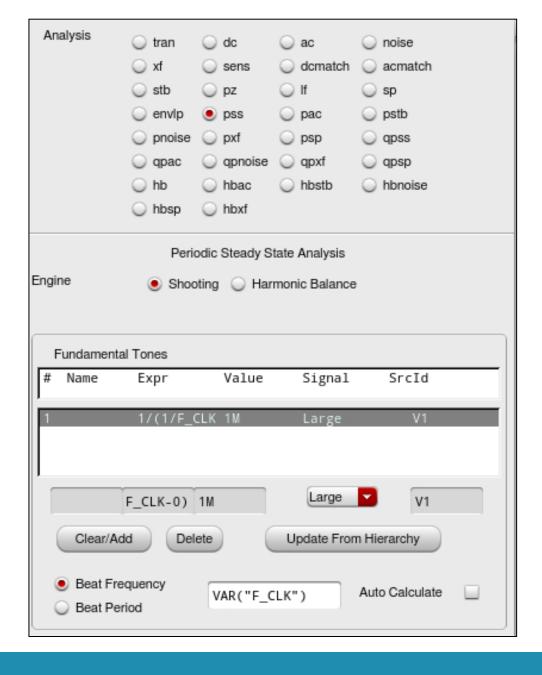
- 1. Add PSS analysis
- 2. Shooting engine
- 3. Beat Frequency:
  - It's the period in which PSS perform analysis
  - Set equal to clock frequency variable
  - Or: Auto Calculate (will be same result)




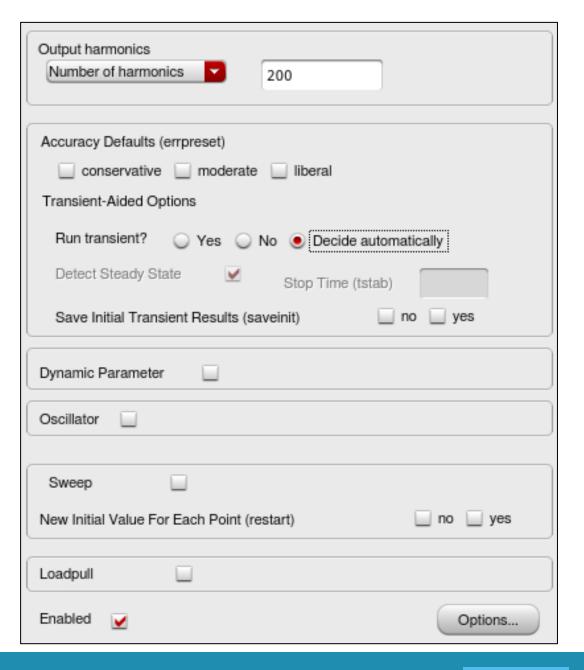
### PSS setup (3)

- Make number of harmonics into
   100's (trade-off with accuracy)
  - It sets the f<sub>MAX</sub> considered by PSS
  - Above a certain amount, it will make no difference anymore (no extra noise)
  - Usually, 200 is good enough
- 2. Transient: decide automatically
  - Helps PSS to converge





#### **PNOISE** simulation


- Periodic noise analysis
- It uses the steady-states computed by PSS to find either:
  - A time-average noise spectrum at the output, OR
  - Noise spectrum at the output at specific times
- We want the latter (i.e. after amplification phase)

We integrate the noise spectrum to obtain the RMS noise voltage


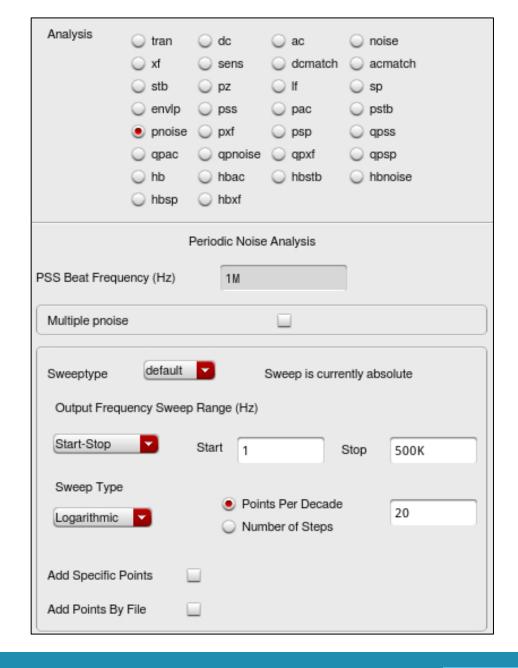
#### PNOISE setup (1)


- PSS Beat Frequency is obtained from PSS sim. setup of the same ADE test
- 2. Set frequency sweep range (for the noise PSD) up to f<sub>s</sub>/2!
  - In this example, 500K = 1M/2
  - Tip: you could also write in the Stop field VAR("F\_CLK")/2, if you have such a variable F\_CLK





### PNOISE setup (2)

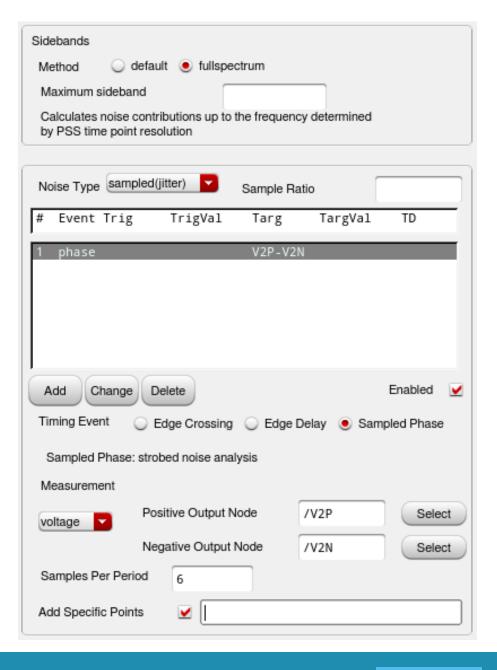
- 1. Method = fullspectrum
  - To make sure you fold all the noise in
  - Keep maximum sidebands empty
- 2. Noise Type = sampled (jitter)
  - We need PSD at specific time!





### PNOISE setup (3)

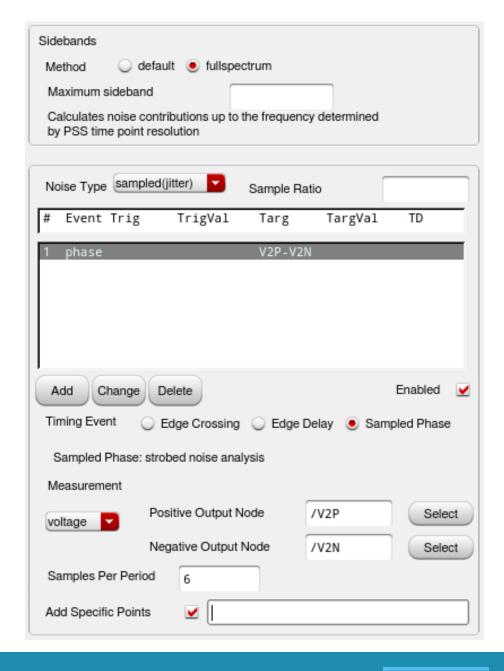
- 1. You will need to set sampling events:
  - Timing Event = Sampled Phase
  - Then select and positive and negative output node
  - Don't use a balun to measure differential noise (buggy)! Select the two diff. nodes of interest
  - Select no. samples per period and/or specific point in time (of the PSS result) where you want the PSD from (re-run later if the timing is off)
- 2. Then press "Add"! The event must be added to the list now
- 3. If you ever change the settings (e.g. samples per period), you **must** press "Change"!




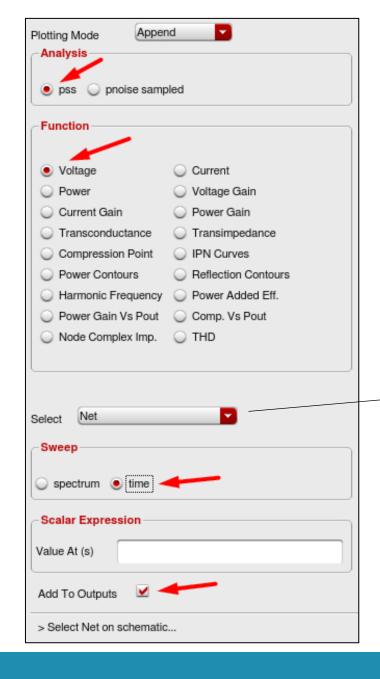
#### Plotting PSS results

- As usual, in ADE use ResultsDirect Plot > Main Form ..
- PSS form: plotting a voltage
   vs. time (in a single period) is
   usually what you do
- Check "Add To Outputs" to add the expression to ADE for future simulations ©




Can also select a differential net if you want!




#### Plotting PNOISE results

#### **Noise Spectrum**

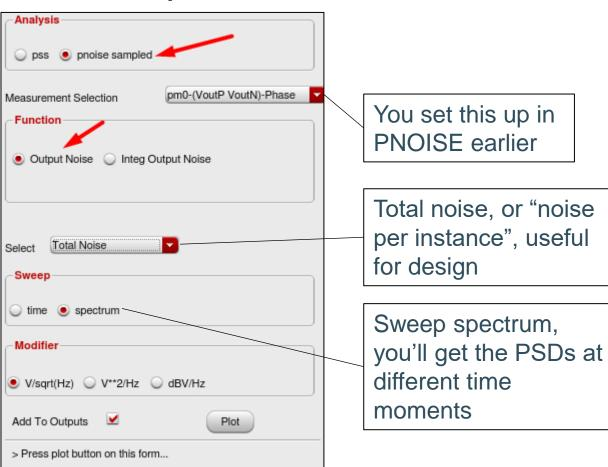


#### **Integrated Noise**

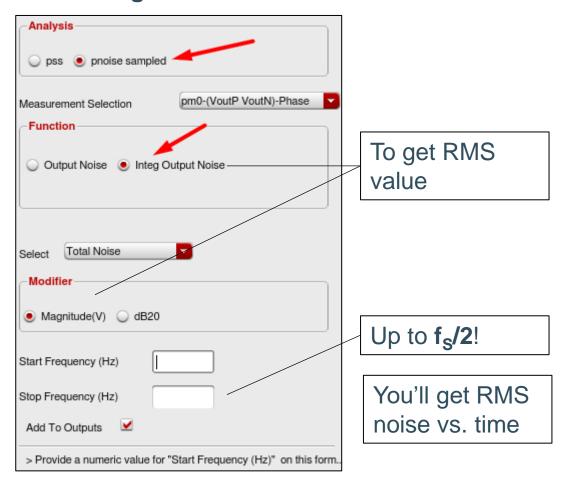



#### Demo 2: "demo\_TH\_NOISE\_TB"

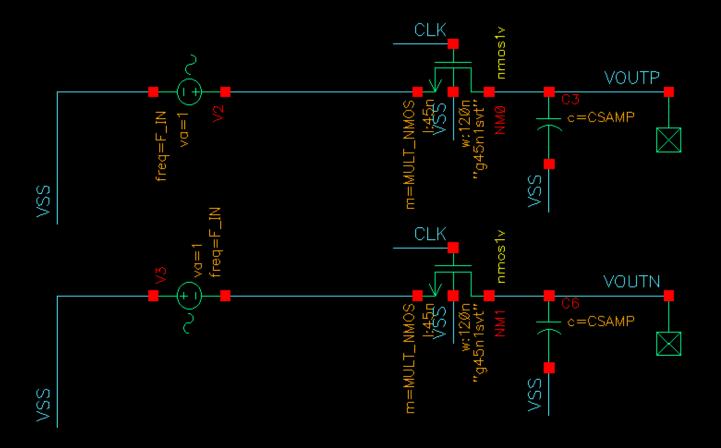

- Differential T/H withtransistors →
- Total sampleddifferential noisepower should be2kT/C


#### Demo 2: Setup


- We've set the sampling cap to 1 pF on each side
  - NMOS multiplier = 1, f<sub>CLK</sub> = 10 MHz ⇔ shouldn't matter much
  - Expected single-ended RMS noise voltage is sqrt(kT/C) = 64 uV<sub>RMS</sub>
  - Expected differential RMS noise voltage is sqrt(2kT/C) = 90.5 uV<sub>RMS</sub>

- PSS, PNOISE are setup properly
- Setup and results are on next slides




#### Demo 2: Setup

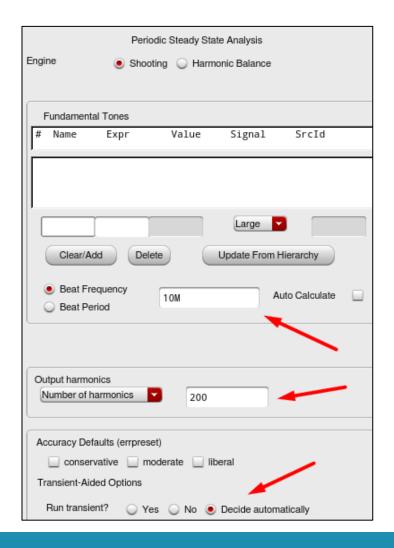


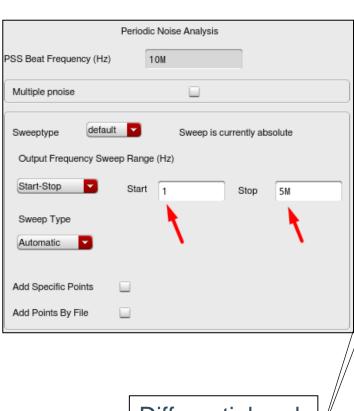

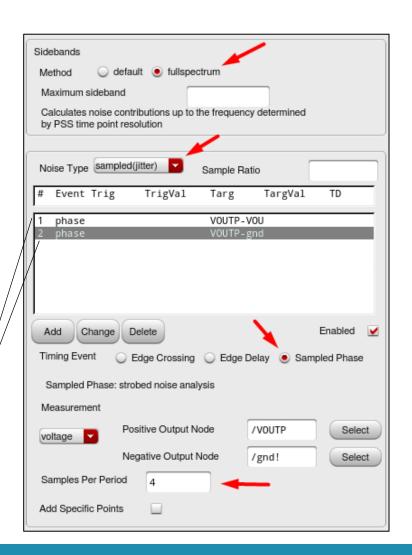Differential and single-ended measurements





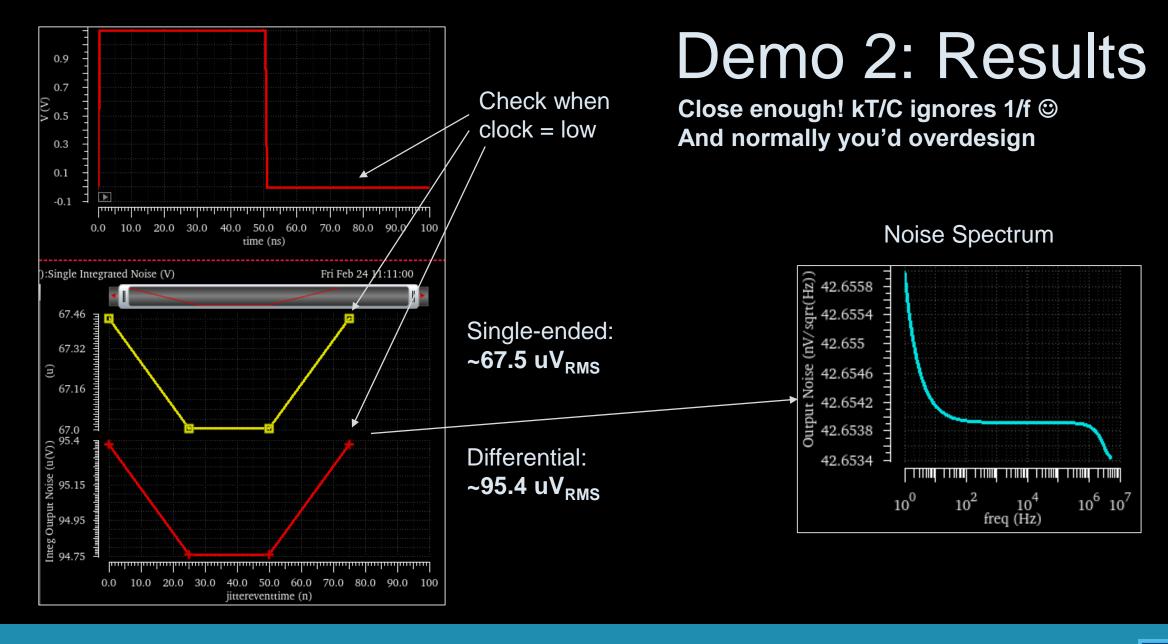



#### Demo 3: "demo\_SCAmplifier\_PNOISE\_TB"

- To showcase how you would simulate noise in your DAMSIC project. Setup is very similar to demo 2!
- Important notes (see ADE):
  - Made fin = 0, Vin = 0 (via design variables)
  - Output baluns are disable in the schematic (else PNOISE becomes buggy)
  - Switching frequency is 70 MHz, so PNOISE and integral up to 35 MHz



#### Demo 3: setup

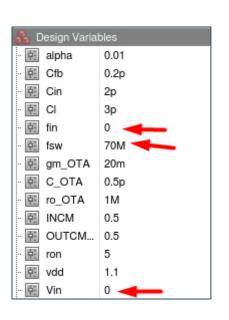


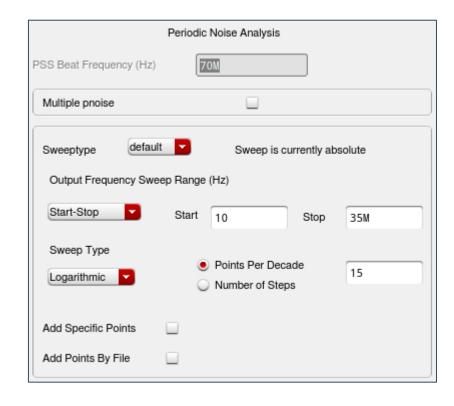





#### Demo 3: results

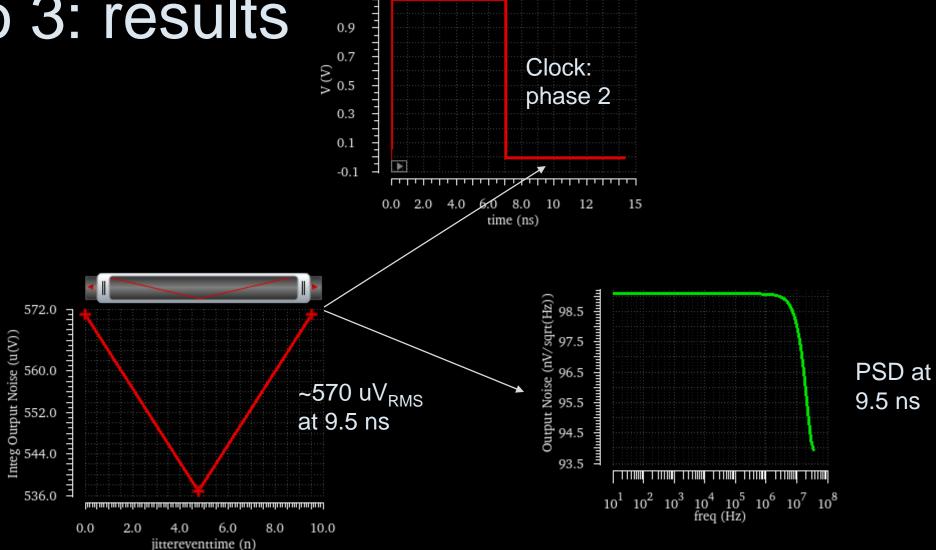



### PSS + PAC SIMULATION SETUP AND DEMO



#### Static settling error $\Leftrightarrow$ PAC

- PAC = periodic AC simulation
- It's a way to find your switched-cap amplifier's AC response

- PAC uses PSS to see the average voltage gain at the output ©
  - remember, normal AC sim. considers only one steady state
- you can check the DC-gain of the switched-cap. 
   ⇔ static settling error!
  - PAC = alternative to long-duration transient simulation



#### Demo 4: "demo\_SCAmplifier\_PAC\_TB"

Almost same setup as demo 3, now PSS + PAC

#### Schematic:


Input source must have a PACmagnitude now (equal to 1)

#### ADE:

- Lower switching frequency to ~100k, you are interested in low-f effects
- Enable PAC simulation (see setup on next slide) → sidebands = 0!





#### Demo 4: schematic setup

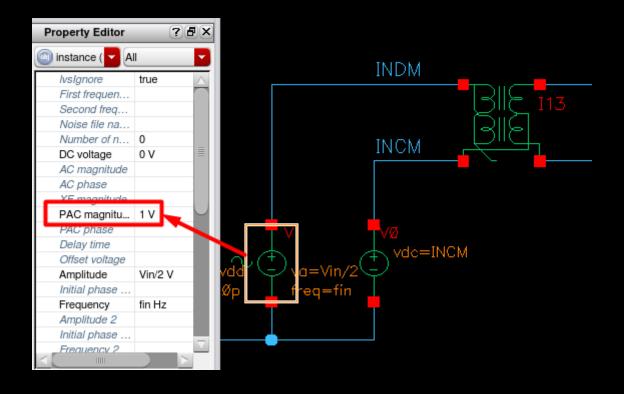


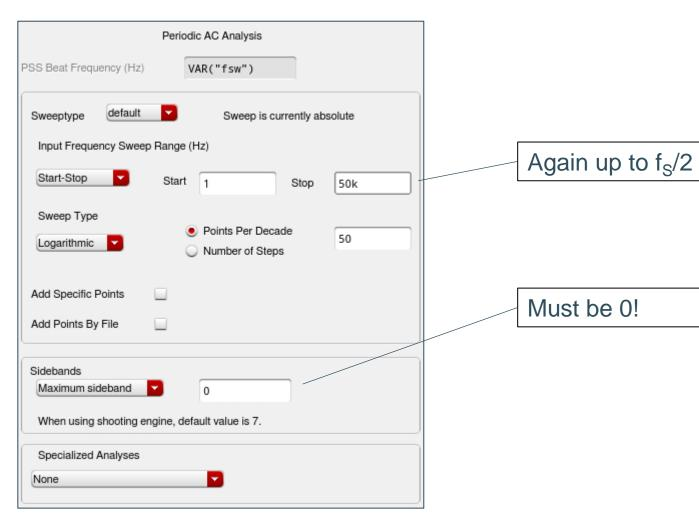
## PAC setup + plotting (Direct Plot Form)



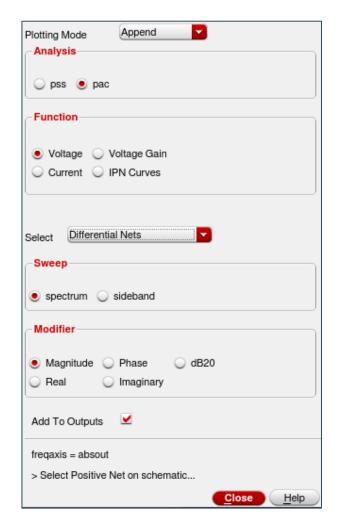



#### Demo 4: results

